



Introduction to Power Electronics

Buck DC-DC Converter

Department of Engineering Science (DES)

Faculty of Innovation Engineering (FIE)

Macau University of Science and Technology (M.U.S.T.)

Presenter: SUN Chuan




Date: Thur., Sept. 05, 2024



Introduction to Power Electronics

What is Power Electronics?



William E. Newell's Description

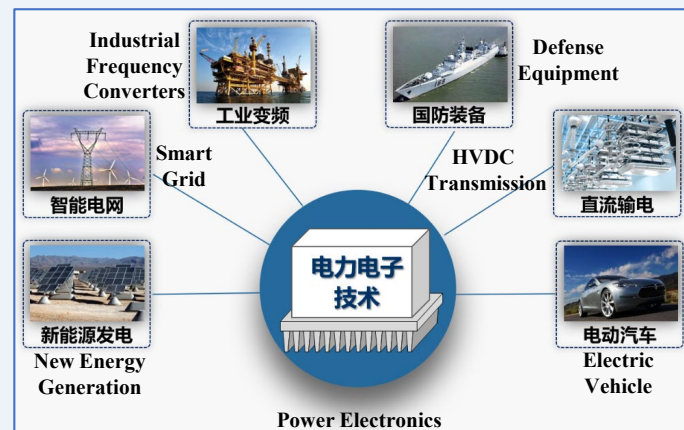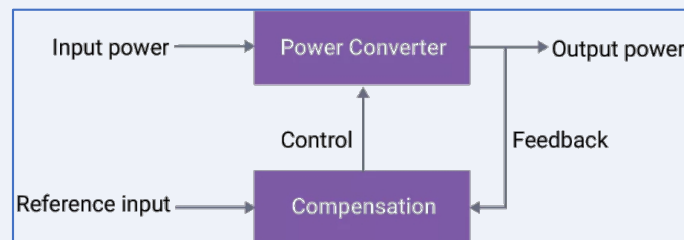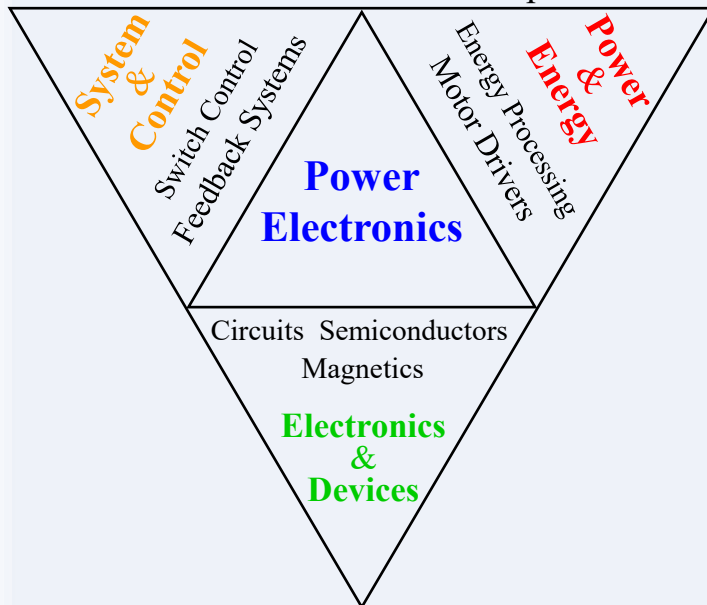

Source: <https://sicpower.fudan.edu.cn/26999/list.htm>

The **Power Electronics Technology** consists of a cross-section of the disciplines of *electricity*, *electronics* and *control theory*. It uses power semiconductor devices as switching elements, thereby controlling or modifying the voltages or currents for energy conversion.

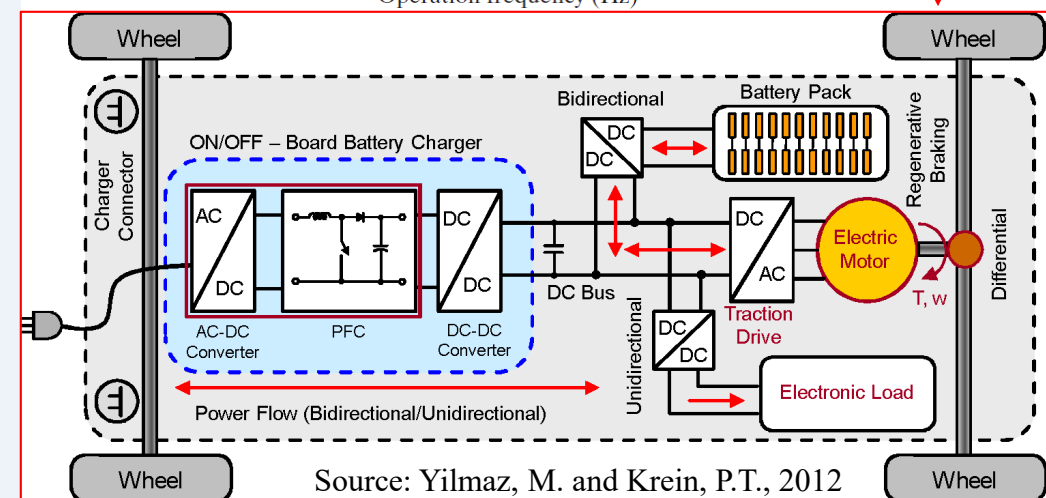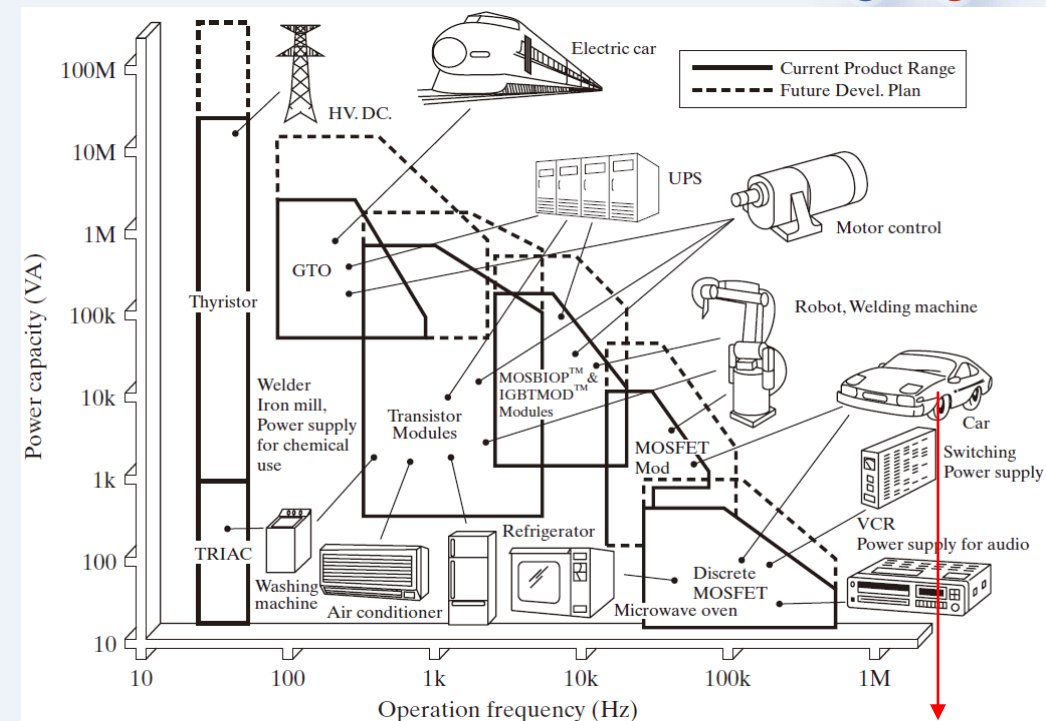
Related Courses for Bachelor of Science in Automation and Systems Engineering [DES]: *Circuit Analysis*, *Analog Circuits*, *Digital Circuits*, *Principles of Automatic Control*, etc.



Source: Yilmaz, M. and Krein, P.T., 2012


Conventional Solution

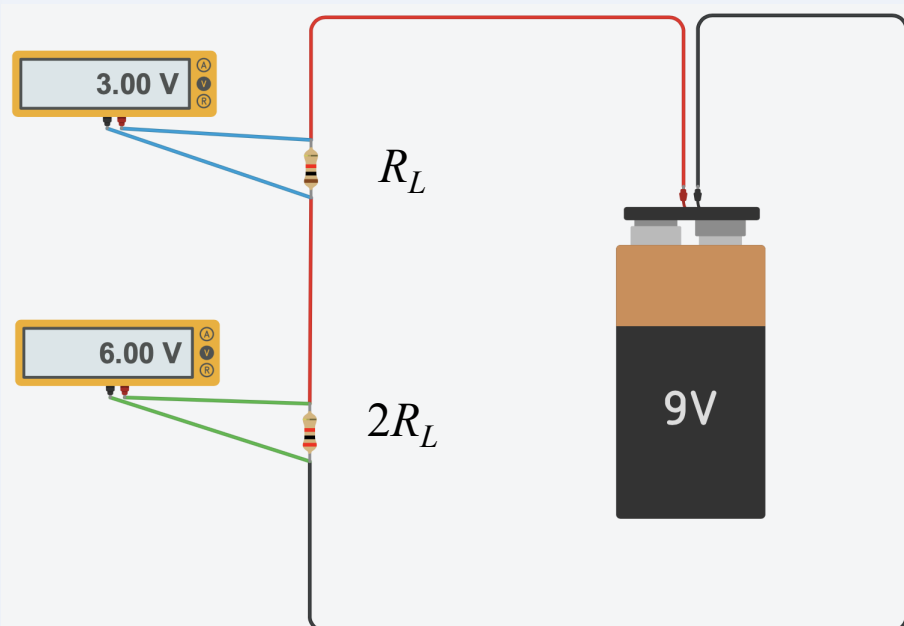How to get a 3-V dc voltage from a 9-V battery?



One simple solution is to use a **Voltage Divider**.

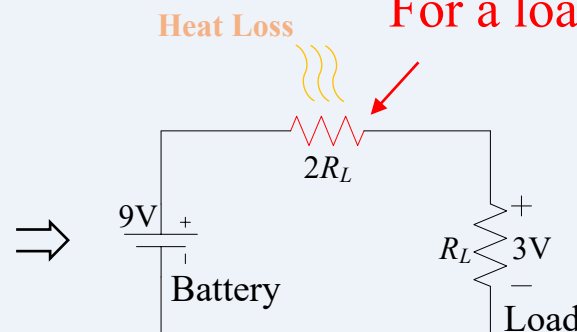For a load resistor R_L , inserting a series resistor $2R_L$.



$$\Rightarrow V_o = V_{in} \times \frac{R_L}{R_L + 2R_L} = 9V \times \frac{1}{3} = 3V$$

Tips:

- Using Ohm's Law for Series Circuits With Multiple Resistors
- The total voltage drop is equal to the sum of the individual voltage drops across all resistors.



Problems with the Voltage Divider

- ☹️ ■ **Low Efficiency:** The power absorbed by the $2R_L$ resistor is twice as much as delivered to the load and is lost as **heat**, making the circuit only **33.3 percent efficient**.
- ☹️ ■ If the value of the load resistance changes, the output voltage will change unless the $2R_L$ resistance changes proportionally.

Power Electronics Solution



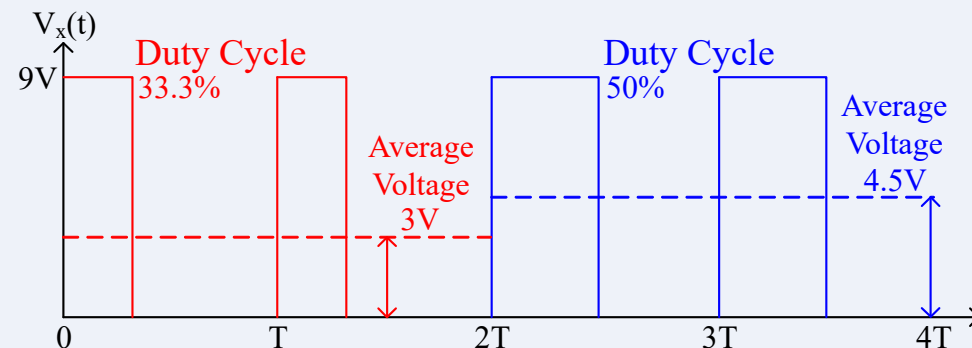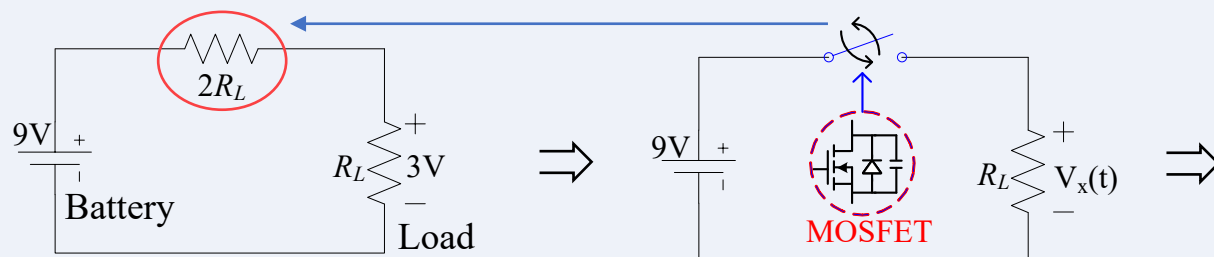
To use a MOSFET in place of the $2R_L$ resistance



The switch is opened and closed periodically. When it is closed $V_x = 9V$, and when it is opened $V_x = 0V$.

NOTE: The square waveform V_x can be expressed as a **Fourier series** containing a **dc term** (i.e., **average value**) plus sinusoidal terms.
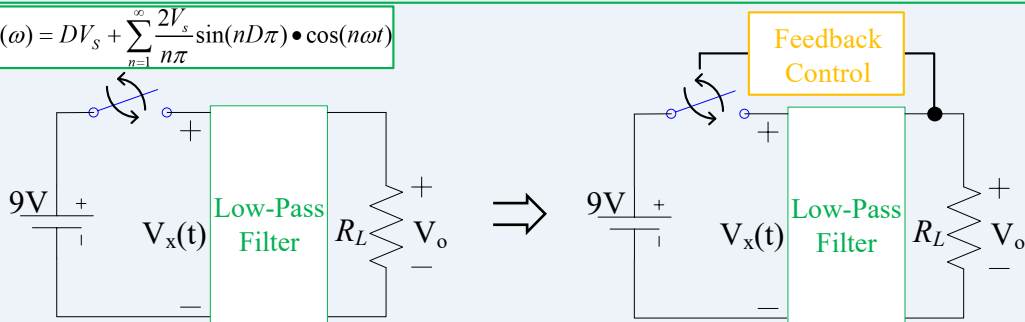
$$V_{EO}(\omega) = DV_s + \sum_{n=1}^{\infty} \frac{2V_s}{n\pi} \sin(nD\pi) \bullet \cos(n\omega t)$$



- A low-pass filter can remove the ac terms of V_x
- A feedback control system can detect the output voltage and adjust the switch's duty cycle to maintain the desired output.

The average value of V_x : $avg(V_x) = \frac{1}{T} \int_0^T V_x(t) dt = 9D$

Duty Cycle $\rightarrow D$


If $D=33.3\%$, $avg(V_x) = 3V$

If $D=50\%$, $avg(V_x) = 4.5V$

Advantages of Power Electronics Circuit

- 😊 **High Efficiency:** Ideally, the power absorbed by the switch is zero, making the circuit **100 percent efficient**.
- 😊 **Easy for Use:** The load voltage can be changed easily by adjusting the duty cycle. With feedback control, the output voltage can be maintained regardless of R_L .

A Practical Buck Converter

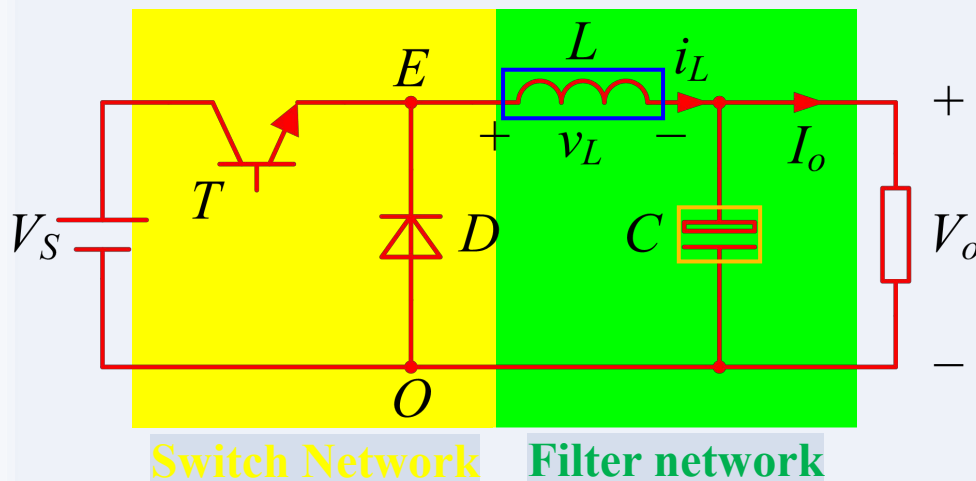

LC Second-Order Low-Pass Filter

$$V_L = L \frac{di_L}{dt} \rightarrow i_L = \frac{1}{L} \int V_L dt + I_{L0}$$

L can control current and store energy




$$i_C = C \frac{dv_C}{dt} \rightarrow v_C = \frac{1}{C} \int i_C dt + V_{C0}$$

C can smooth voltage and store energy

Why is diode necessary in a practical buck converter?

Inductor's current cannot suddenly change!

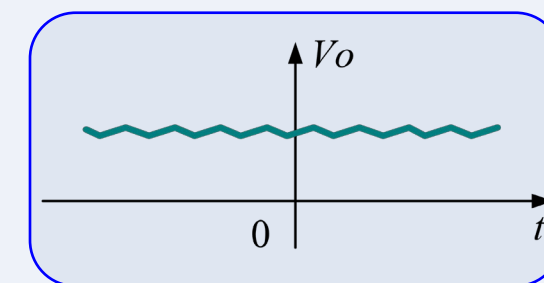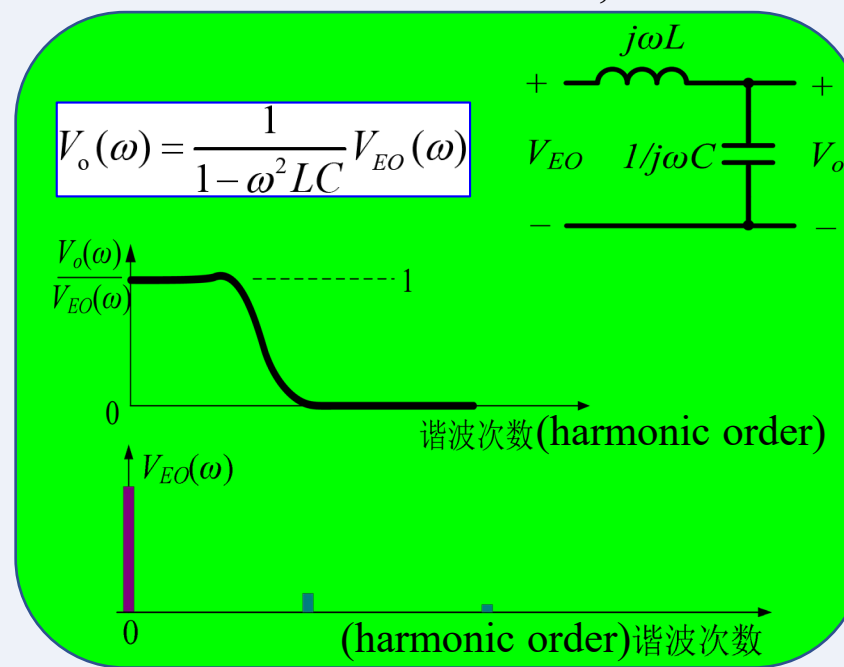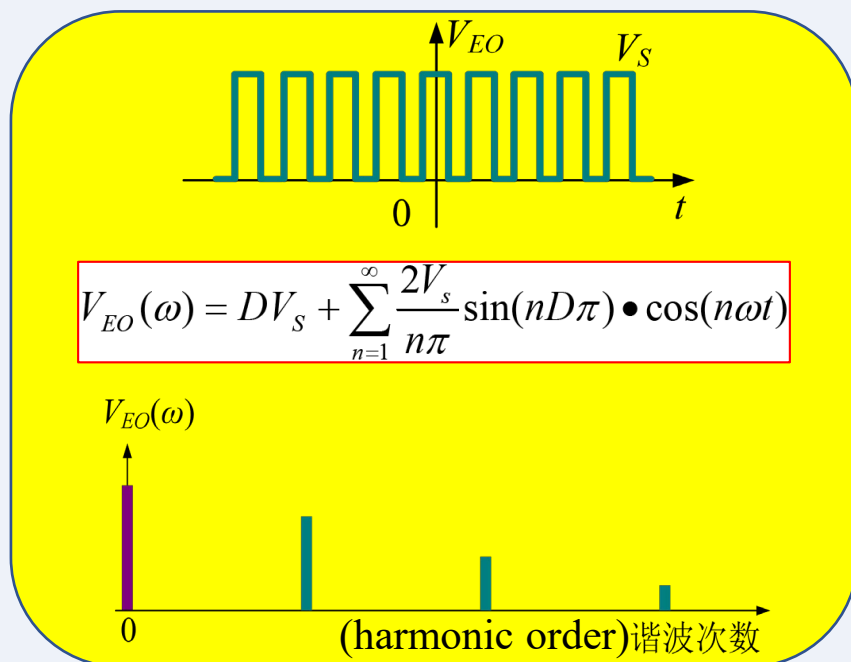When switch is turned off, the diode can take over the inductor's current.




Output Voltage with Ripples

Buck Converter: Continuous Conduction Mode (CCM)




Switch T is Turned on

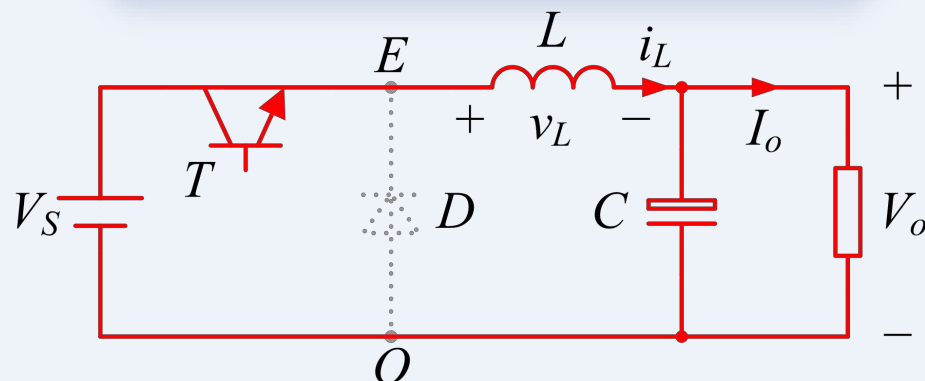

$$v_L = V_S - V_o = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{V_S - V_o}{L}$$

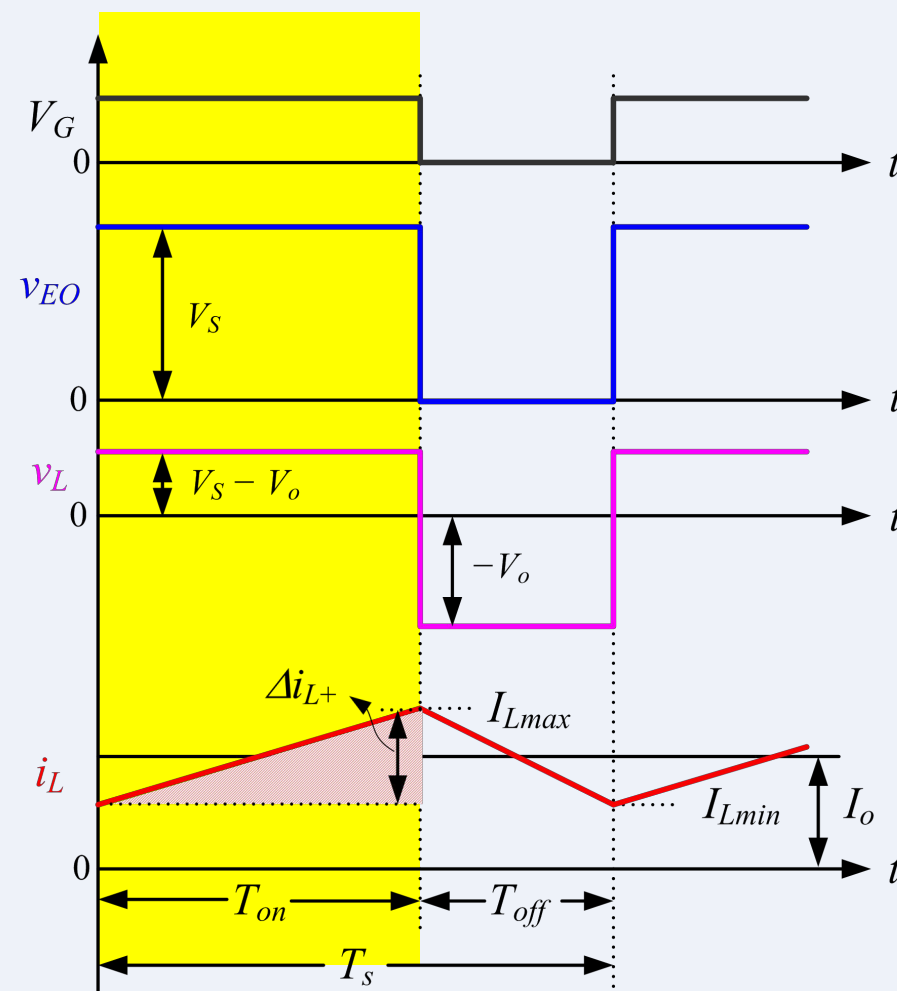
$$\Delta i_{L+} = \frac{V_S - V_o}{L} \cdot T_{on}$$



Buck Converter: Continuous Conduction Mode (CCM)




Switch T is Turned off

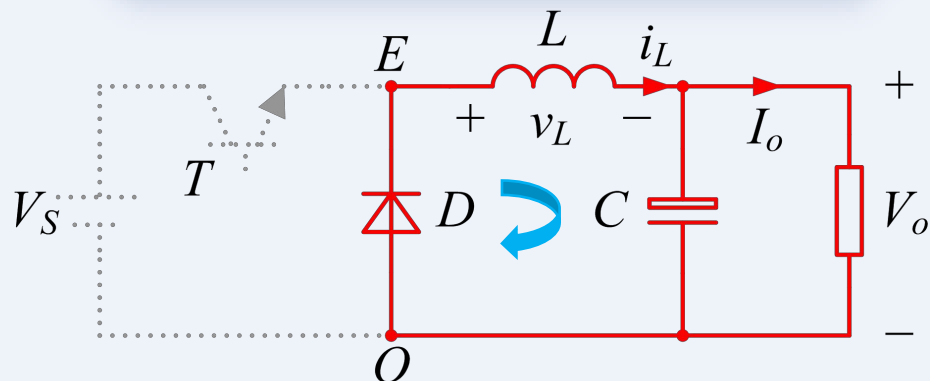

$$v_L = -V_o = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{-V_o}{L}$$

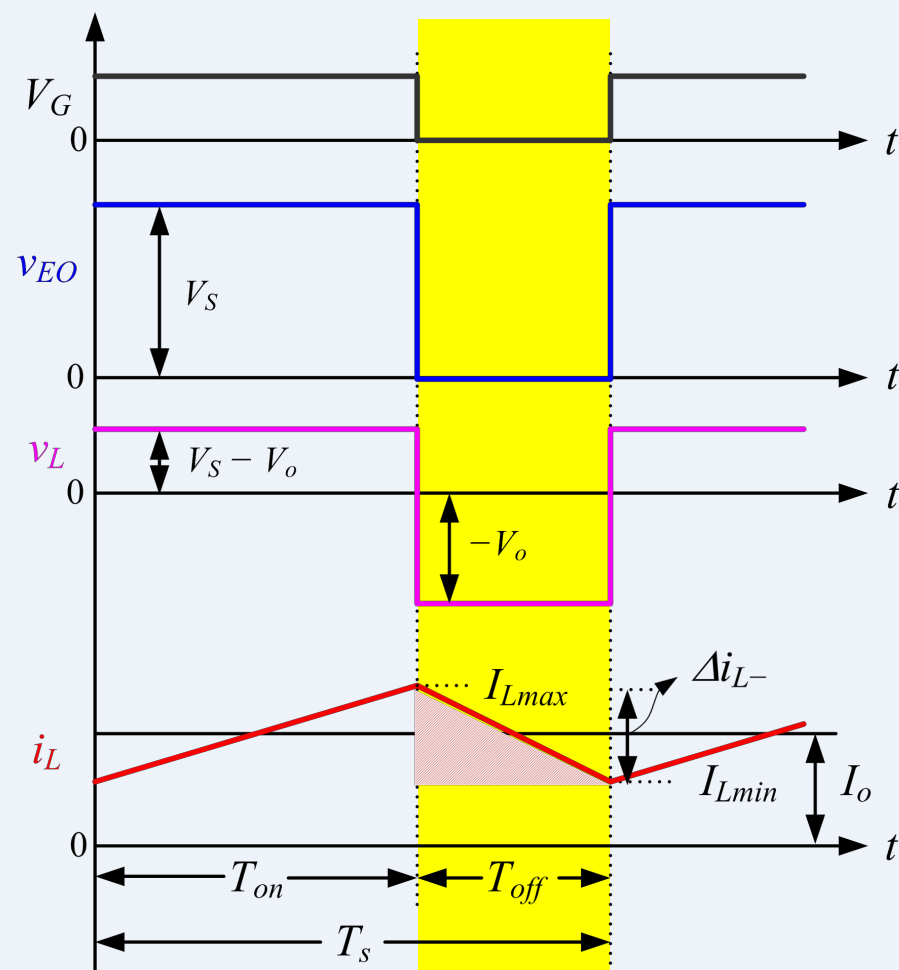
$$\Delta i_{L-} = -\frac{V_o}{L} \cdot T_{off}$$



Buck Converter: Principal of Volt-Second Balance



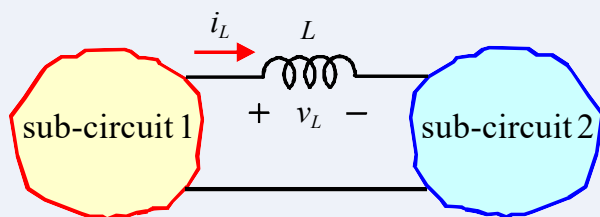Principal of Inductor Volt-Second Balance




$$i(t_0 + T) - i(t_0) = \frac{1}{L} \int_{t_0}^{t_0 + T} v_L(t) dt = 0$$

$$\text{avg}[v_L(t)] = V_L = \frac{1}{T} \int_{t_0}^{t_0 + T} v_L(t) dt = 0$$

➤ For periodic currents, the average voltage across an inductor is zero.

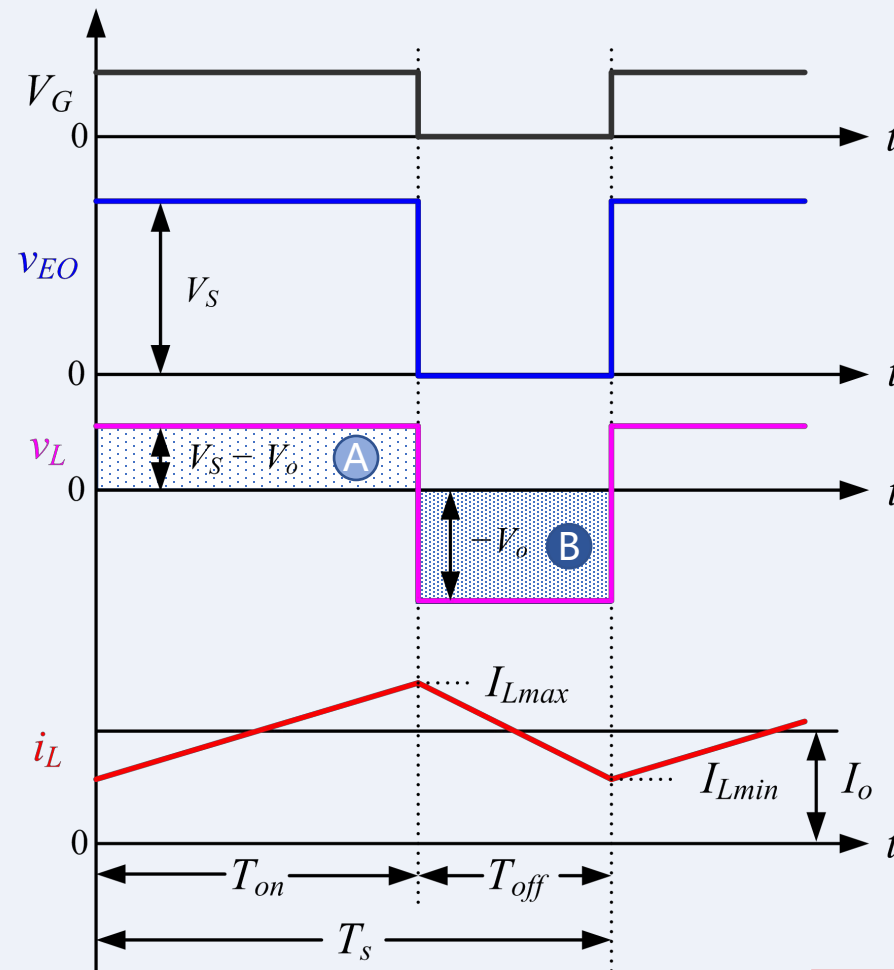Otherwise, the average current will increase or decrease continuously, thus damaging the inductor.



Step-by-Step Derivations:

$$\Delta i_{L+} + \Delta i_{L-} = 0$$

$$\Delta i_{L+} = \frac{V_s - V_o}{L} \cdot T_{on}$$

$$\Delta i_{L-} = -\frac{V_o}{L} \cdot T_{off}$$


$$\frac{V_s - V_o}{L} \cdot T_{on} - \frac{V_o}{L} \cdot T_{off} = 0$$

$$\frac{V_o}{V_s} = \frac{T_{on}}{T_{on} + T_{off}} = \frac{T_{on}}{T_s} = D$$




For a Buck converter: Controlling V_o by D

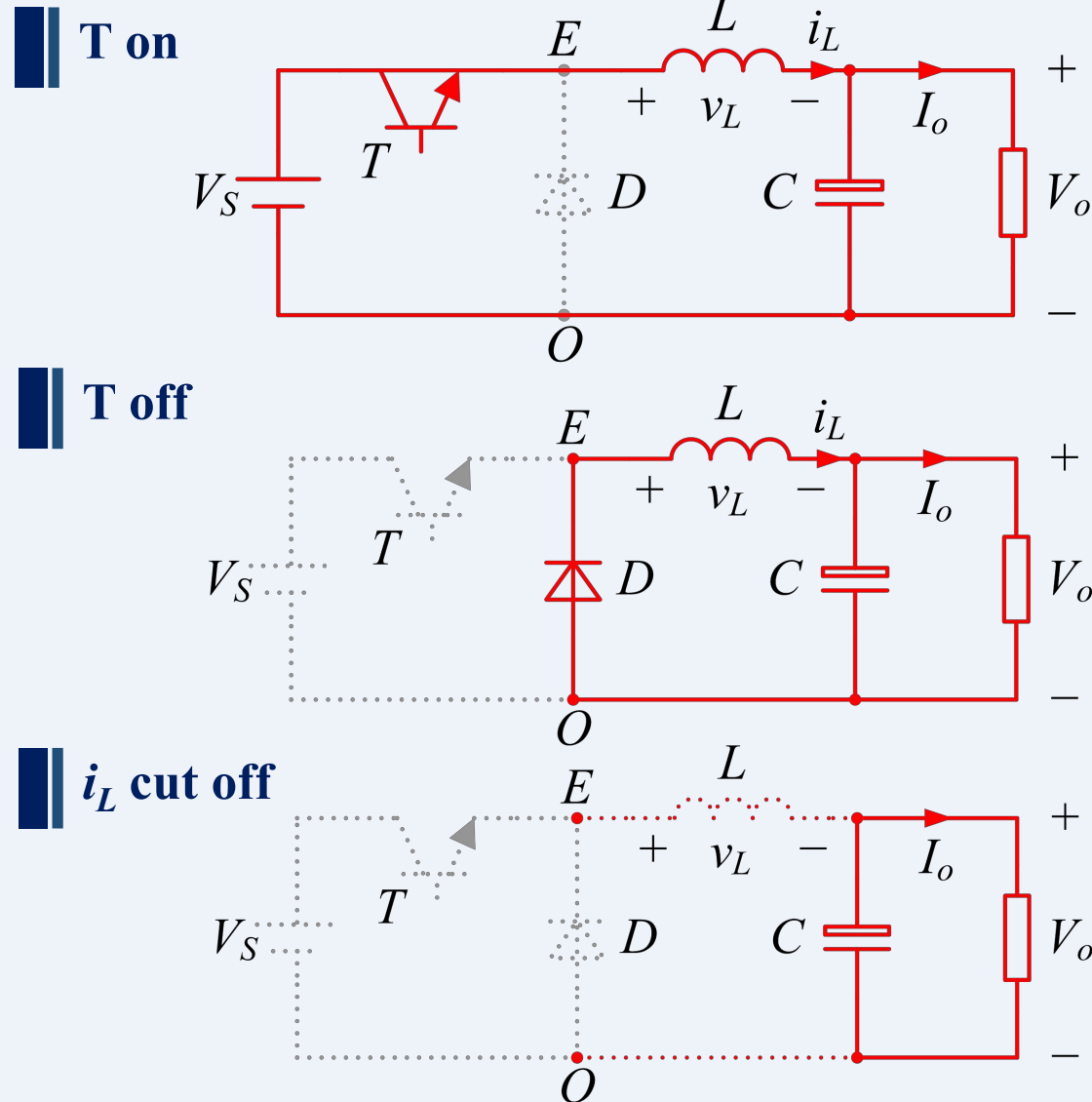Buck Converter: Discontinuous Conduction Mode (DCM)



Classroom Test


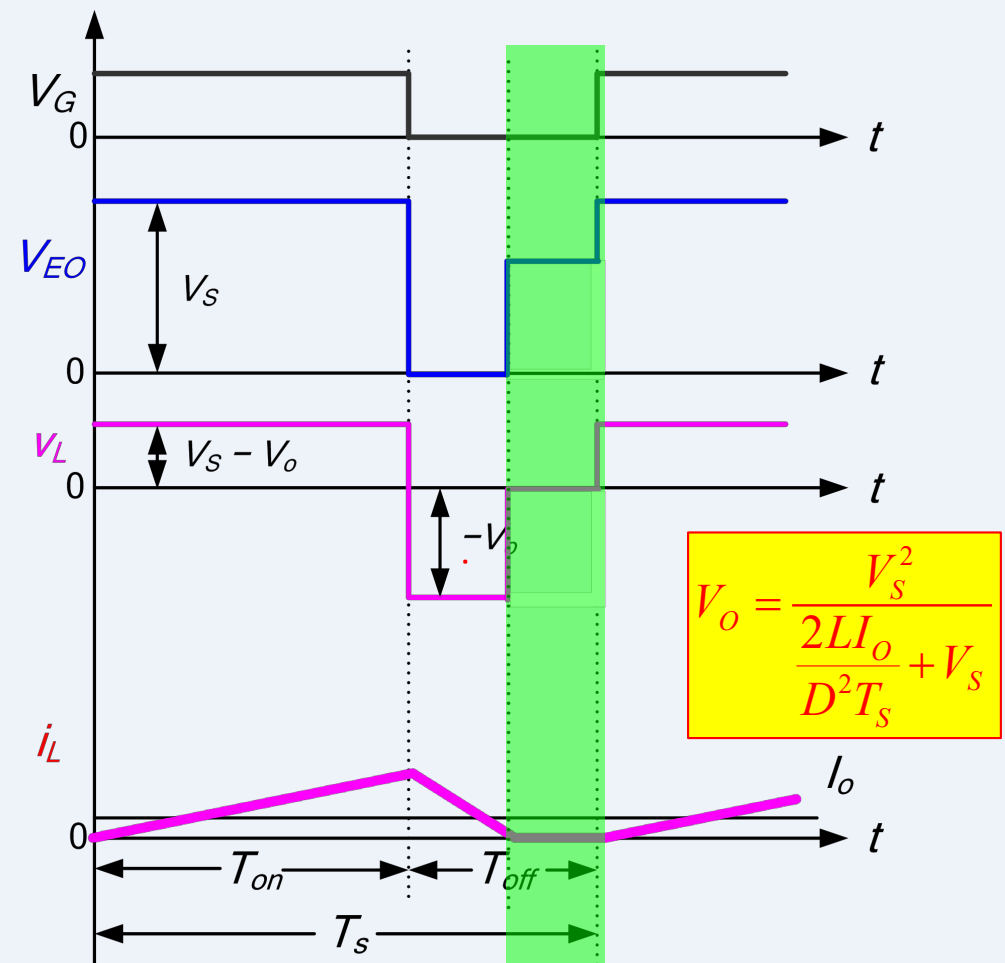
Try to calculate the relationship between input and output voltages under DCM mode.



Buck Converter: Summary

- A switched-mode dc-dc converter is much more efficient than a voltage divider because of reduced losses in the switch.
- A buck converter has an output voltage less than the input.
- Practical buck converters typically contain two semiconductors (a diode and a MOSFET) and two energy storage elements (a capacitor and an inductor in combination).
- The output voltage of a buck converter can be adjusted by the duty cycle.
- The principle of inductor volt-second balance states that the average value, or dc component, of voltage applied across an ideal inductor winding must be zero.
- Through appropriate parameter design, a buck converter can always work in CCM.

Buck Converter Simulation in PLECS®

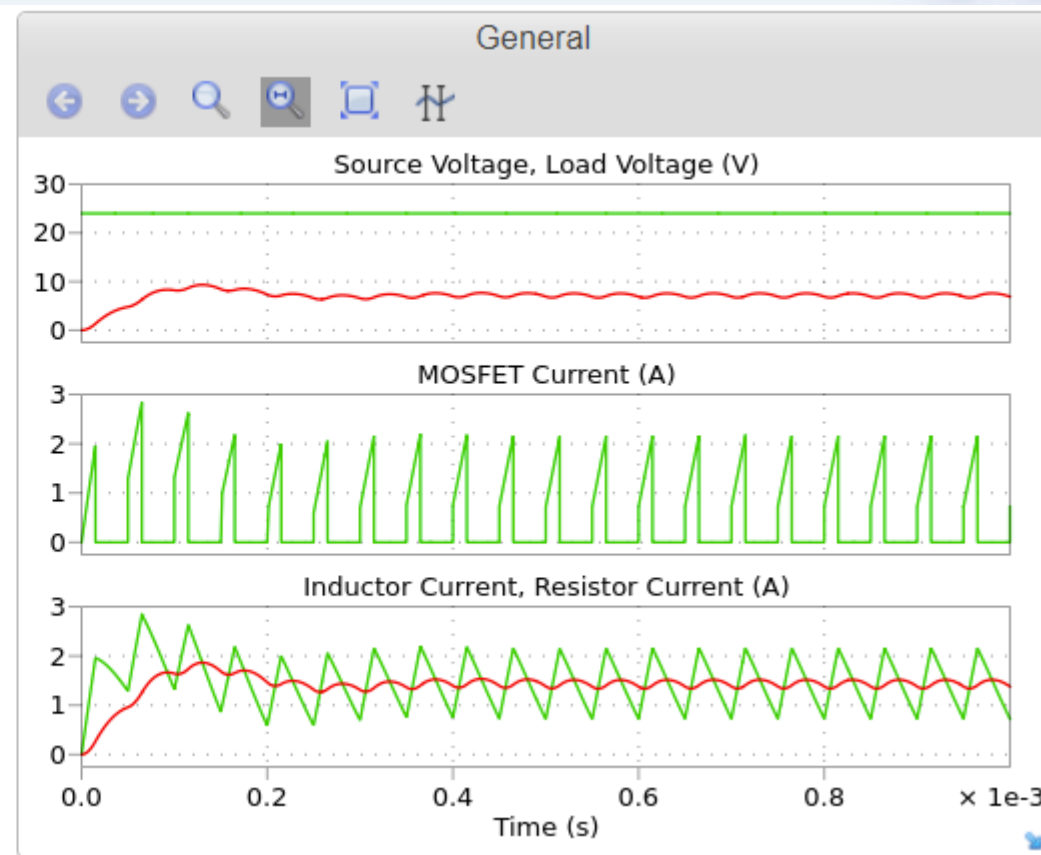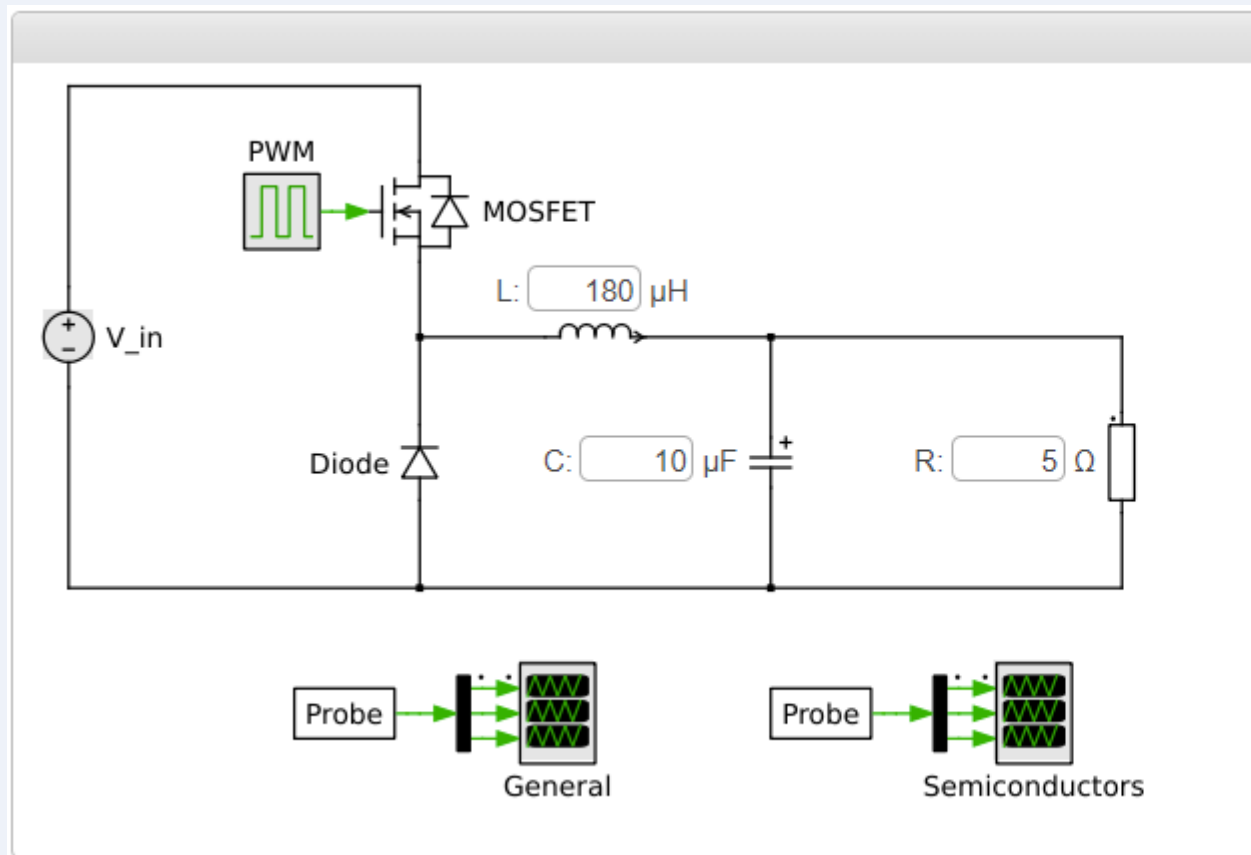


Simulation powered by **PLECS** using WebSIM patented technology

<https://www.plexim.com/de/academy/power-electronics/buck-conv>


Exercises:

- ❑ Change the PWM duty cycle of the converter from 0.3 to 0.5 and observe how the average output voltage changes from 7.2 V to 12 V.
- ❑ Change the resistance value from 5 Ω to 50 Ω and observe how the converter goes into discontinuous conduction mode.

Experiments of Buck Converter

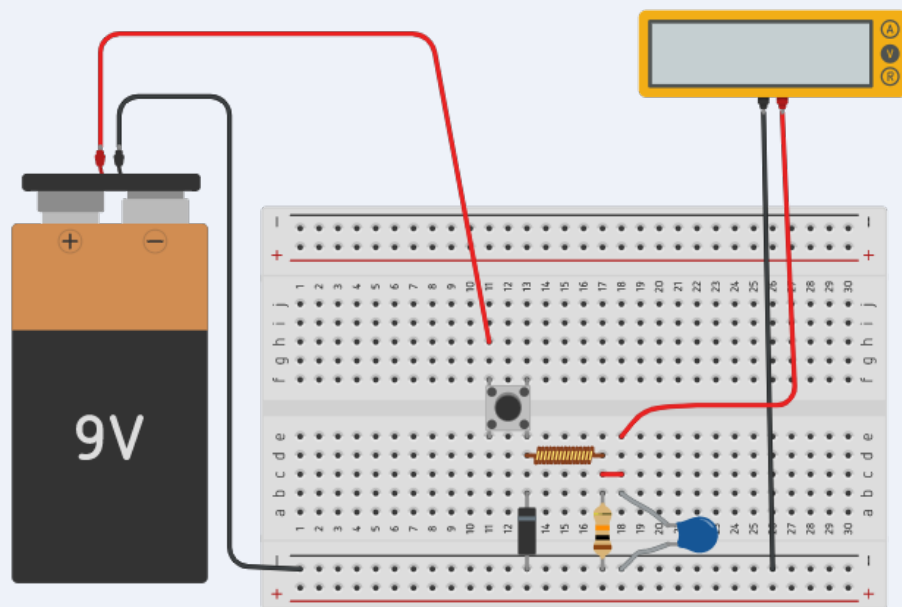

Buck Converter With Push Button

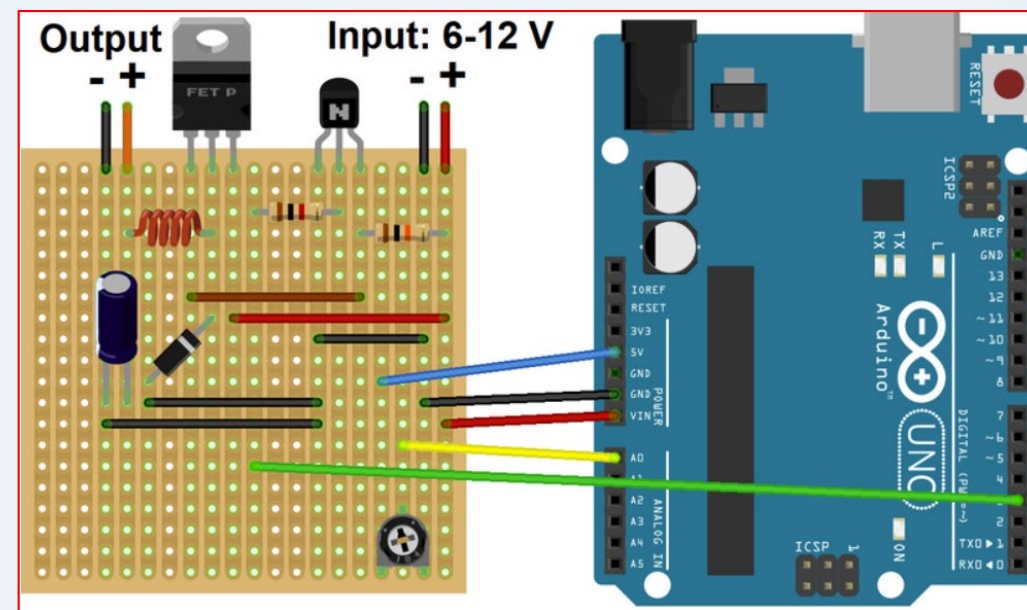

Buck converter using Arduino for PWM Generation

Source: https://samiralavi.github.io/blog/buck_coverter/buck_converter_arduino/


Report in Groups

Your hand-written report must include the following:

- A short introduction to Buck DC-DC converters
- Detailed steady-state analysis calculation of the Buck converter
- Experimental results (plots and tabulated data) and discussion
- Simulation results (plots and tabulated data) and discussion
- Conclusions


Duty Cycle	Output Voltage		Output Current		Inductor Current	
	Measured	Calculated	Measured	Calculated	Measured	Calculated
10%						
20%						
30%						
40%						
50%						

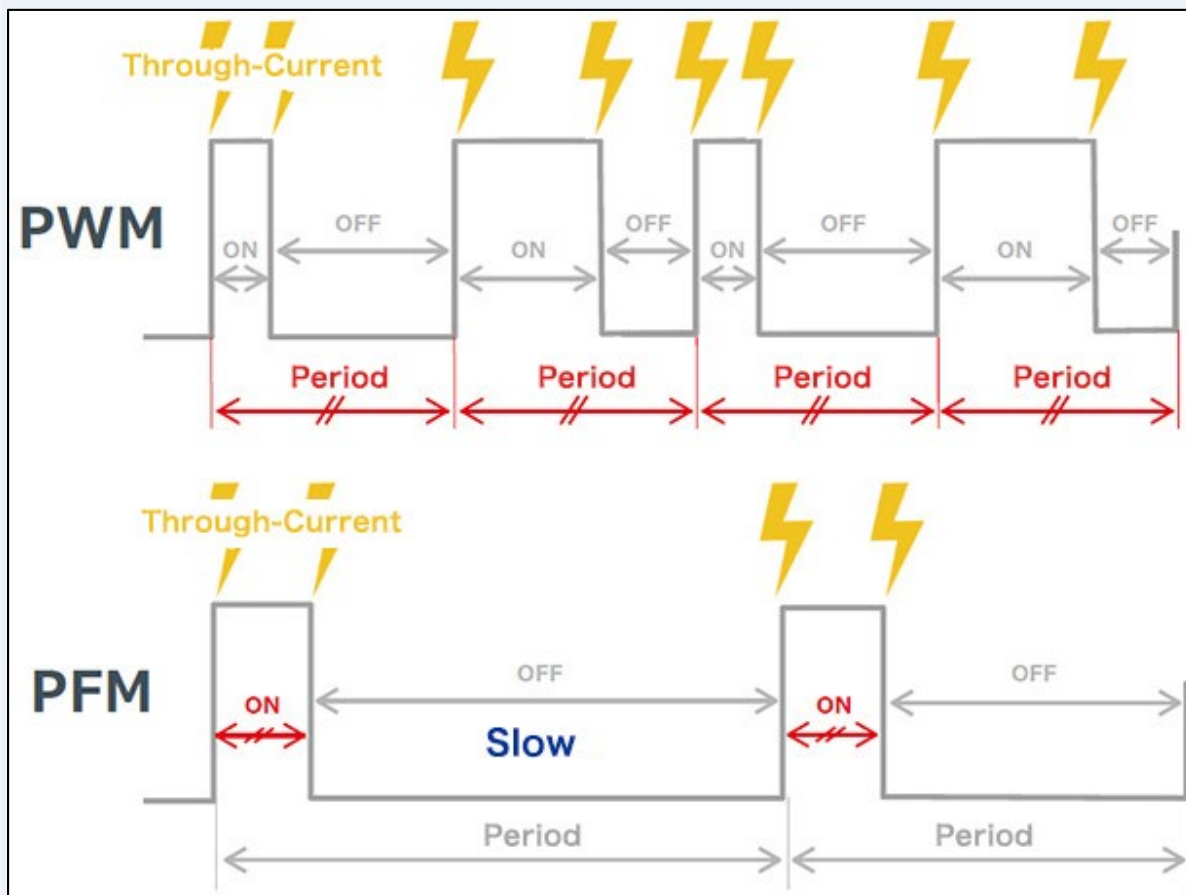Other Modulation Schemes for Buck Converter



■ PWM (Pulse Width Modulation)

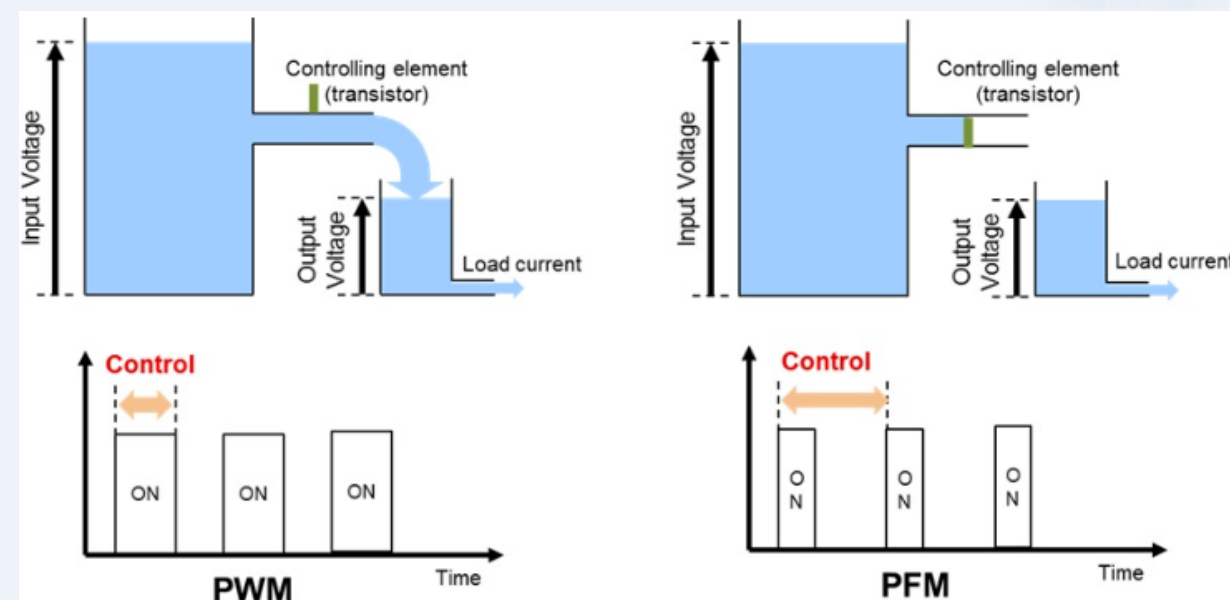A control method that produces the output equivalent from the input voltage at a constant frequency by turning the switch ON.




■ PFM (Pulse Frequency Modulation)

A method for generating the equivalent output by changing the frequency (OFF time) while keeping the ON time constant. There is also a type that varies the ON time while keeping the OFF time constant.

Extracurricular Reading Materials

- [1] W. -R. Liou, M. -L. Yeh and Y. L. Kuo, "A High Efficiency Dual-Mode Buck Converter IC For Portable Applications," in IEEE Transactions on Power Electronics, vol. 23, no. 2, pp. 667-677, March 2008.
- [2] A. Morra, M. Piselli, M. Flaibani and A. Gola, "A buck converter operating in PFM mode, mathematical model and simulation analysis," INTELEC 07 - 29th International Telecommunications Energy Conference, Rome, Italy, 2007, pp. 23-26.

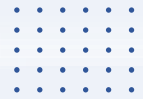

THANK YOU VERY MUCH
FOR YOUR TIME AND ATTENTION !

Questions and Answers